



Information Technology Institute

Digital Circuits


Lab 1

Submitted by:

Ali Yehia Abdelmonem

Design Report


1. Overview of Design

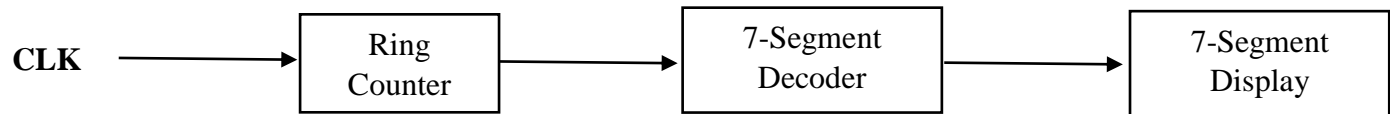

2. Components Used

1. D-Flip Flops
2. AND, OR and NOT Gates
3. Input Logic
4. Clock Source
5. 7- Segment Display

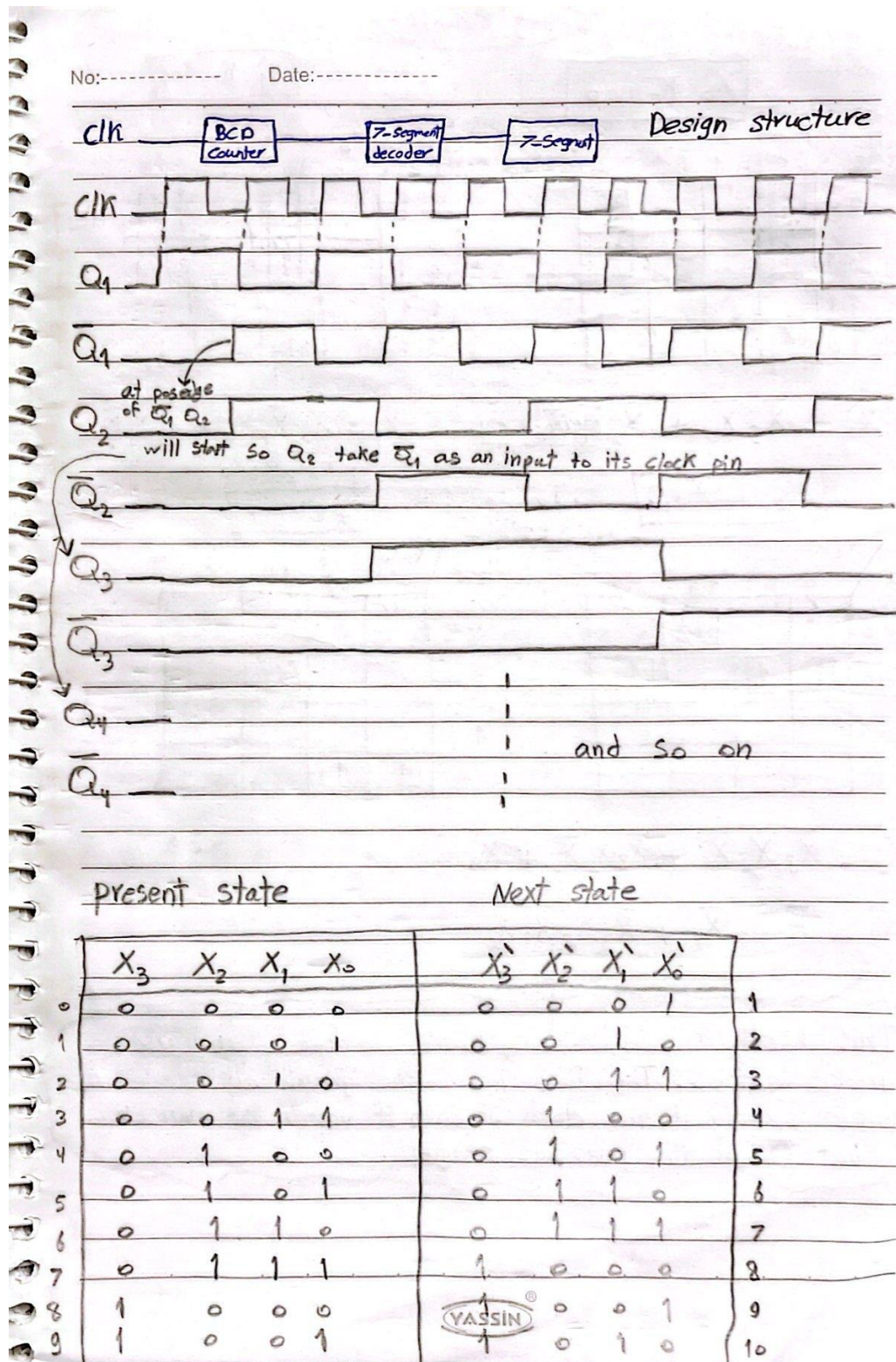3. Step-by-step Description of the Design Process



Ring Counter

No: _____ Date: _____

X_0 K-map

X_1 K-map

$X_3 X_2$ \ $X_1 X_0$	00	01	11	10
00	1			1
01	1			1
11				
10	1			

$X_3 X_2$ \ $X_1 X_0$	00	01	11	10
00		1		1
01		1		1
11				
10		1		

$$X_0 = \bar{X}_3 \bar{X}_0 + \bar{X}_2 \bar{X}_1 \bar{X}_0$$

$$X_1 = \bar{X}_2 \bar{X}_1 X_0 + \bar{X}_3 X_1 \bar{X}_0 + \bar{X}_2 \bar{X}_1 X_0$$

X_2 K-map

X_3 K-map

$X_3 X_2$ \ $X_1 X_0$	00	01	11	10
00			1	
01	1	1		1
10				
11				

$X_3 X_2$ \ $X_1 X_0$	00	01	11	10
00				
01			1	
11				
10	1	1		

$$X_2 = \bar{X}_3 X_2 \bar{X}_1 + \bar{X}_3 X_2 \bar{X}_0 + \bar{X}_3 X_2 X_1 X_0$$

$$X_3 = \bar{X}_3 \bar{X}_2 \bar{X}_1 + \bar{X}_3 X_2 X_1 X_0$$

This method is harder, more complex and uses more gates. Therefore from the graph all needed are FlipFlops only if the clock of each FF wasn't the main clk but \bar{Q} of the previous stage.

No:-----

Date:-----

7-segment decoder

Similarly From K-map

(a) segment For example "1" 4 corners grouped together

AB \ CD	00	01	11	10
00	1		1	1
01		1	1	1
11	1		1	1
10	1	1		1

$$a = \overline{A}\overline{B}\overline{C} + \overline{A}BD + \overline{A}\overline{D} + \overline{A}C + BC + \overline{B}\overline{D}$$

$$b = \overline{A}\overline{C}\overline{D} + \overline{A}CD + A\overline{C}\overline{D} + \overline{B}\overline{C} + \overline{B}\overline{D}$$

$$c = \overline{A}\overline{C} + \overline{A}D + \overline{C}D + \overline{A}B + A\overline{B}$$

$$d = \overline{A}\overline{B}\overline{D} + \overline{B}CD + \overline{B}\overline{C}D + B\overline{C}\overline{D} + A\overline{C}$$

$$e = AC + AB + C\overline{D} + \overline{B}\overline{D}$$

$$f = \overline{A}\overline{B}\overline{C} + \overline{C}\overline{D} + \overline{B}\overline{D} + \overline{A}\overline{B} + AC$$

$$g = \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B} + AD + \overline{B}C + C\overline{D}$$

4. Screenshots of the Simulation



Figure 1: Start of simulation.



Figure 2: Simulation part 1.

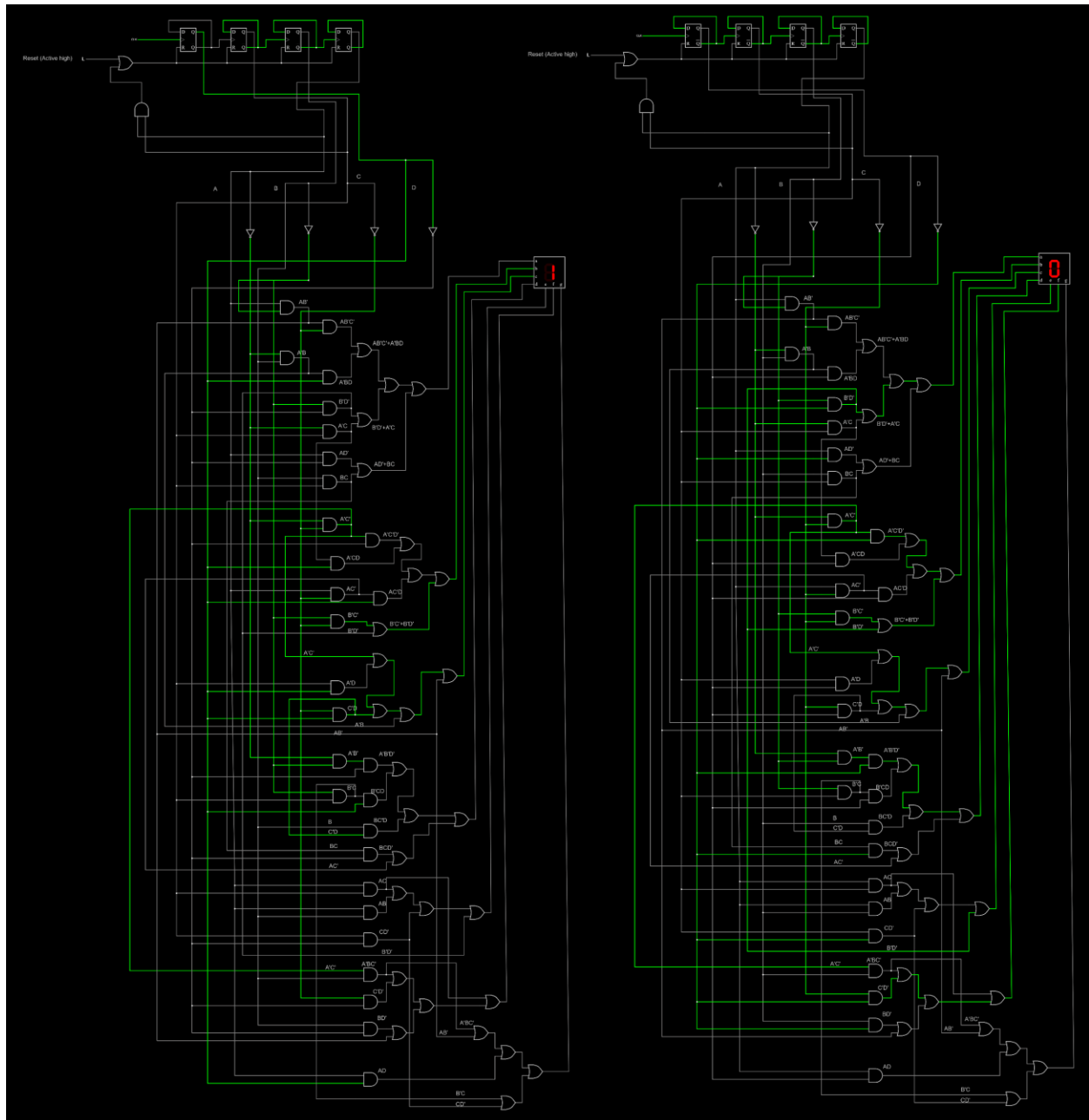


Figure 3: Simulation part 2.



Figure 4: Simulation part 3.

5. Issues Faced

Number 8 is not displayed correctly

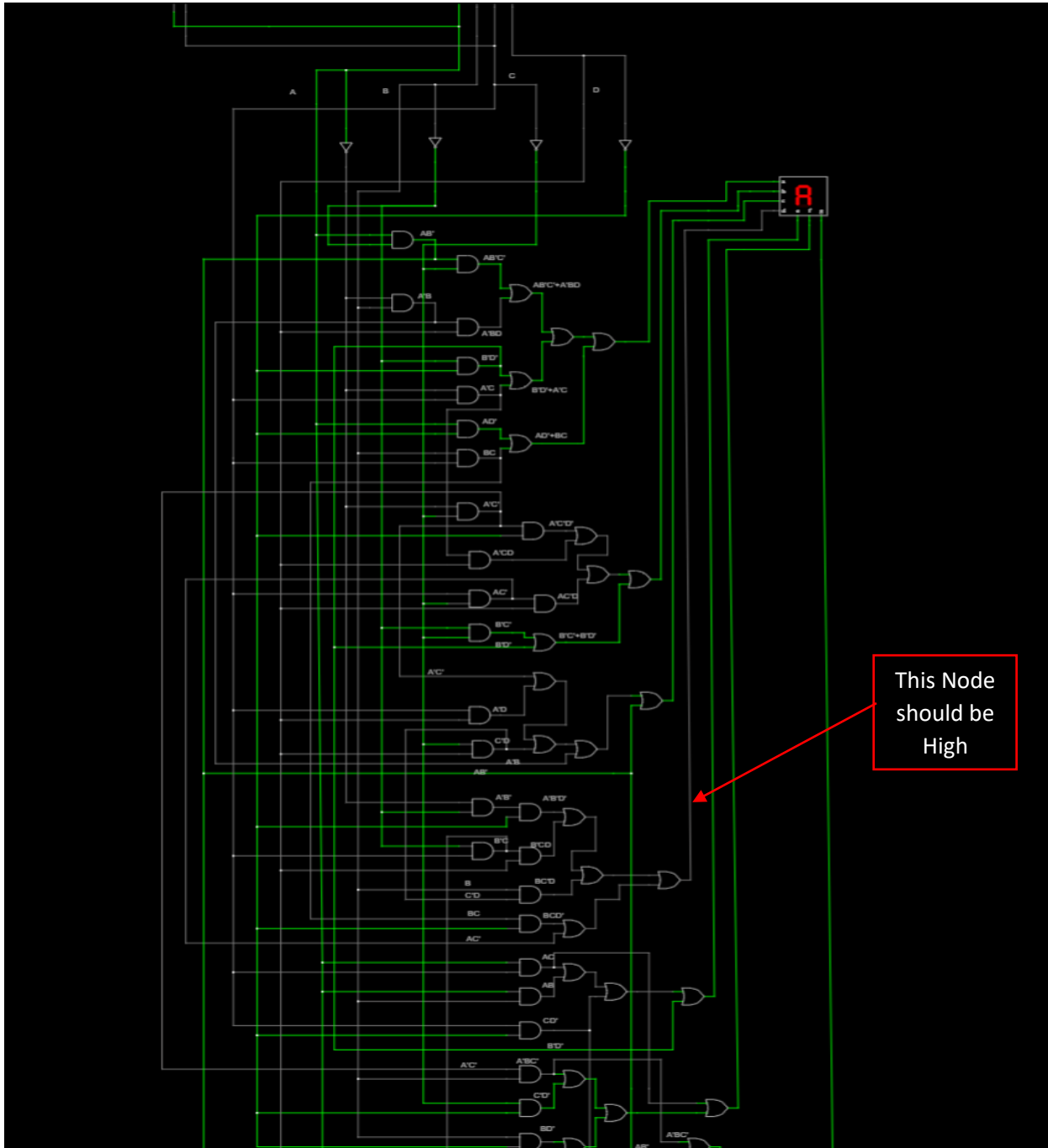


Figure 5: Number 8 not displayed correctly.

According to A B C D truth table:

At number 8 I should have A=1, B=0, C=0, D=0 which is $AB'C'D'$

And (d) segment equation is:

$$d = A'B'D' + B'CD + BC'D + BCD' + AC'$$

Therefore, the argument that must be high to satisfy the high condition for d segment for number 8 will be AC' which is part of $AB'C'D'$ and by checking its node I found out that:

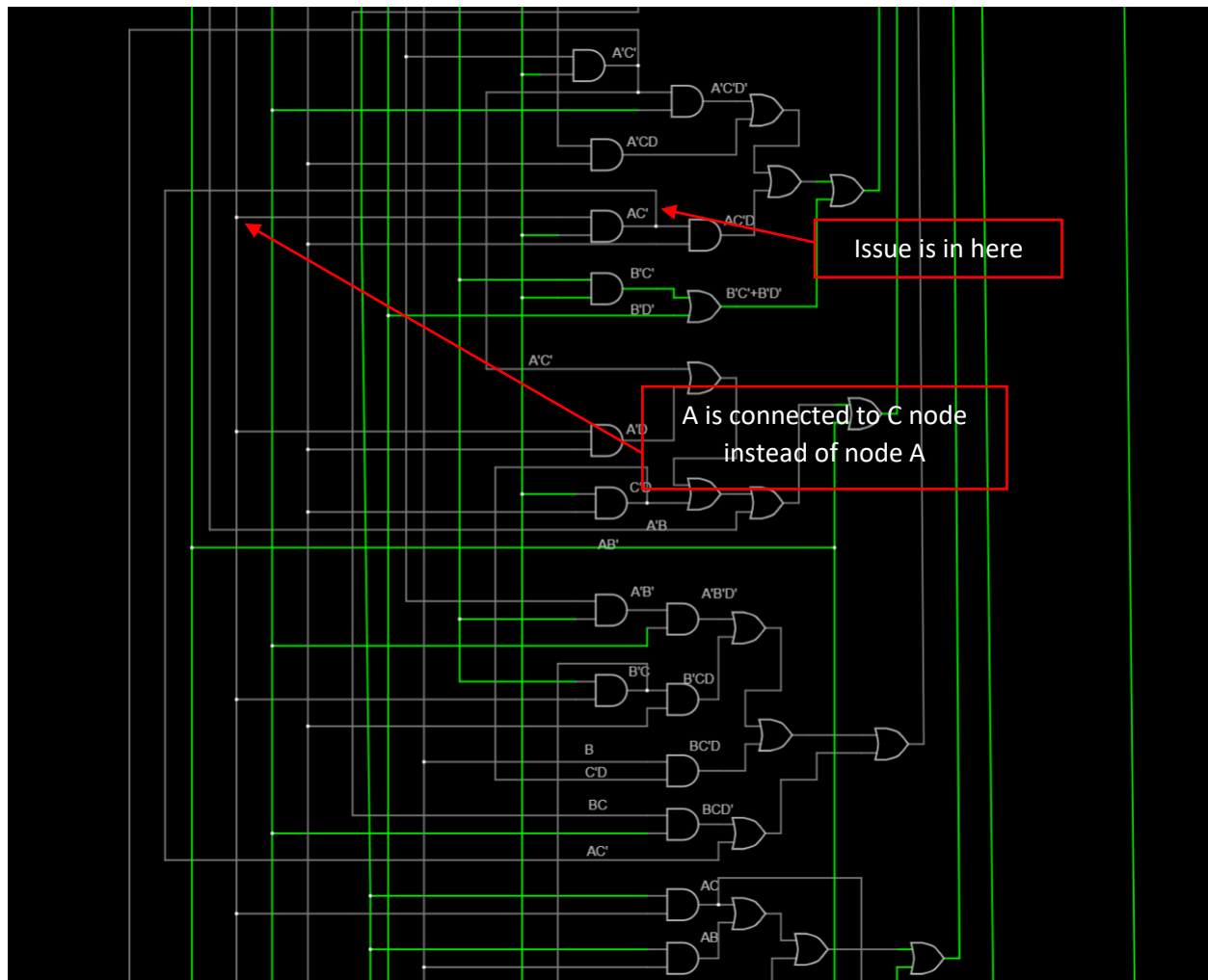


Figure 6: Analyzing and spotting the issue.

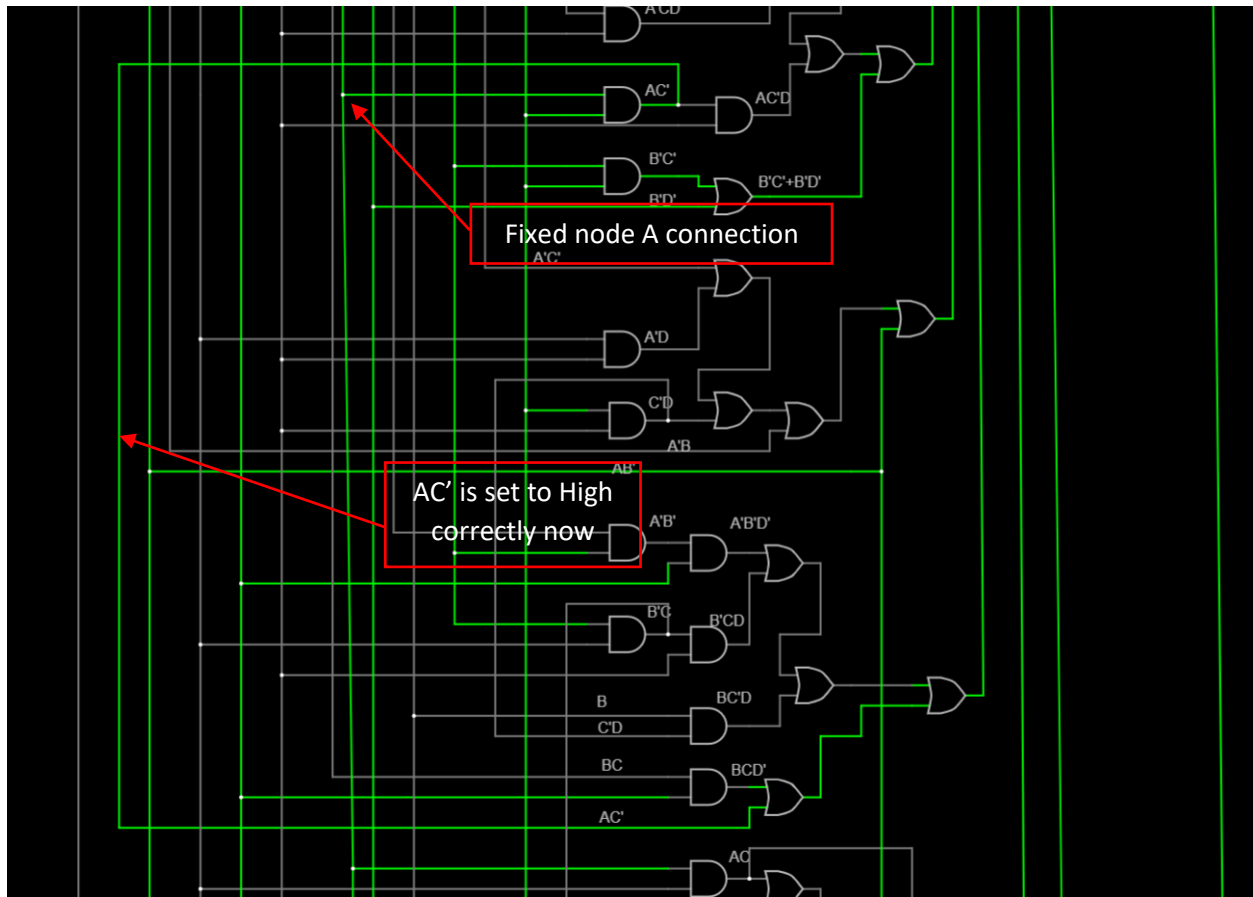


Figure 7: Corrected connection.

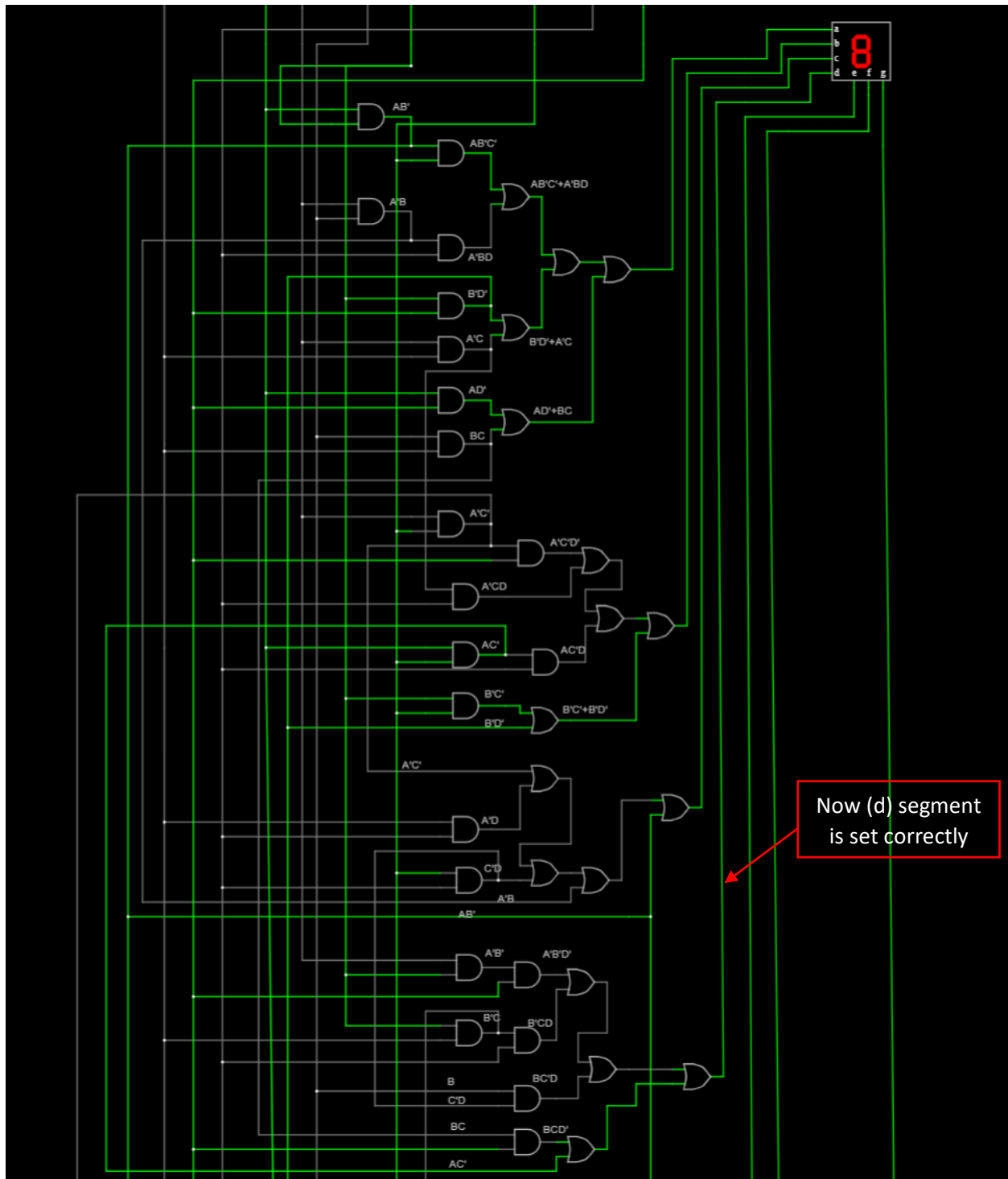


Figure 8: Issue fixed.